

MULTIMEDIA



UNIVERSITY

STUDENT ID NO

--	--	--	--	--	--	--	--	--	--

# MULTIMEDIA UNIVERSITY

## FINAL EXAMINATION

TRIMESTER 1, 2017/2018

### **EEL1166 – CIRCUIT THEORY**

(All Sections / Groups)

14 OCTOBER 2017  
02:30 p.m. - 04:30 p.m.  
(2 Hours)

---

#### INSTRUCTION TO STUDENTS

1. This Question paper consists of 6 pages including cover page and appendix with 4 Questions only.
2. Attempt **ALL FOUR** questions. All questions carry equal marks and the distribution of the marks for each question is given.
3. Please print all your answers in the answer Booklet provided.

**QUESTION 1**

- (a) A bilateral network is shown in Figure Q1(a). Assume that the current flowing through the  $25\ \Omega$  resistor is  $4\text{ A}$ . Find the value of  $V_x$  by using T to  $\pi$  network.  
[10 marks]

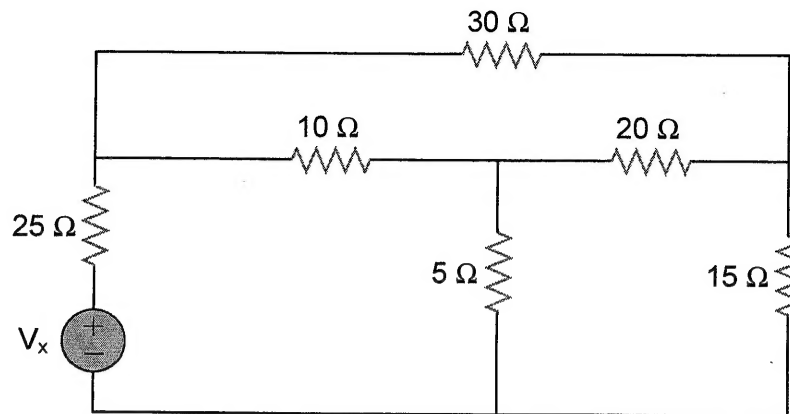


Figure Q1(a)

- (b) Find the power absorbed in the  $8\ \Omega$  resistor in Figure Q1(b) using superposition theorem.

[15 marks]

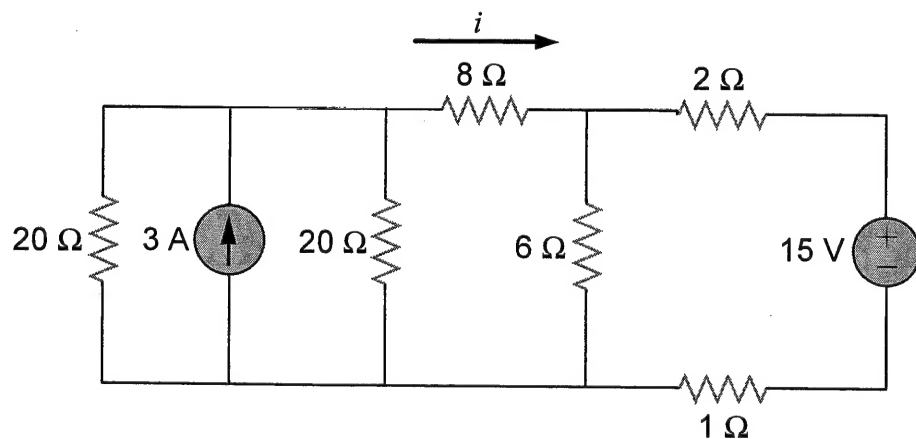


Figure Q1(b)

Continued ...

**QUESTION 2**

(a) For the circuit shown in Figure Q2(a).

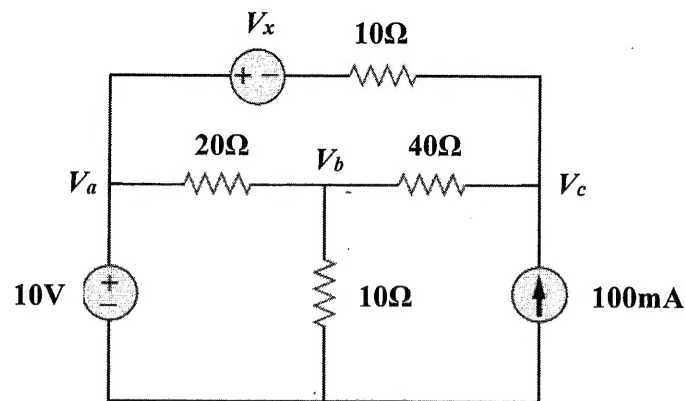


Figure Q2(a)

- (i) State the essential nodes of the circuit. [3 marks]
  - (ii) Convert the unknown voltage source,  $V_x$  branch to current source. [3 marks]
  - (iii) Based on part 2(a)(ii), calculate the node voltages,  $V_a$ ,  $V_b$  and  $V_c$  using nodal analysis if  $V_x = 2V$ . [8 marks]
- (b) Consider the periodic signal,  $Y$  defined by the equations:
- $$Y(t) = \begin{cases} t, & 0 < t \leq 2 \\ 4 - t, & 2 < t \leq 6 \\ -8 + t, & 6 < t \leq 8 \end{cases} \text{ and } Y(t) = Y(t - 8)$$
- (i) Explain why  $Y(t)$  is a periodic, but not an aperiodic signal. [2 marks]
  - (ii) Draw the signal waveform and label clearly the x-axis and y-axis. [3 marks]
  - (iii) Find the period, rms value and crest factor of  $Y$ . [6 marks]

**Continued ...**

**QUESTION 3**

- (a) Apply phasor analysis to evaluate what of  $v(t)$ :  
 $v(t) = 110 \cos(20t + 30^\circ) - 220 \cos(20t + 45^\circ) \text{ V}$

[7 marks]

- (b) In the circuit of Figure Q3 (b), determine the phasor of  $i_s(t)$ . Calculate the average power delivered by the voltage source  $v_s(t)$ .

[12 marks]

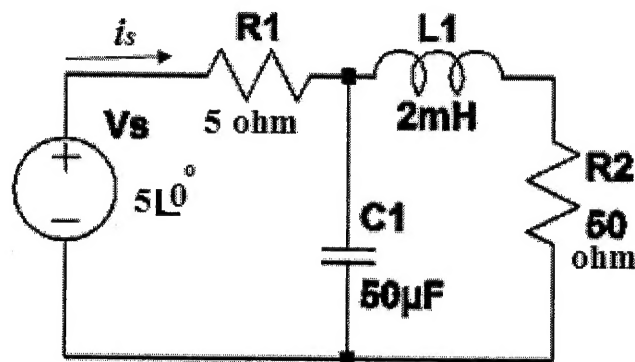


Figure Q3 (b)

- (c) A parallel RLC circuit has resonance at  $f_o = 400 \text{ Hz}$ , has a Q factor of 50 at  $f_o$ , and a resistive branch of  $100 \Omega$ . Determine the values of L and C in the other two branches.

[6 marks]

Continued ...

**QUESTION 4**

- (a) A parallel LR circuit is shown in Figure Q4(a). Given that  $R_s = 8\Omega$ ,  $R_1 = 24\Omega$ ,  $R_2 = 8\Omega$  and  $L = 7H$ , determine the inductance current ( $i_L$ ) for time  $t > 0$  and  $t < 0$ .

[10 marks]

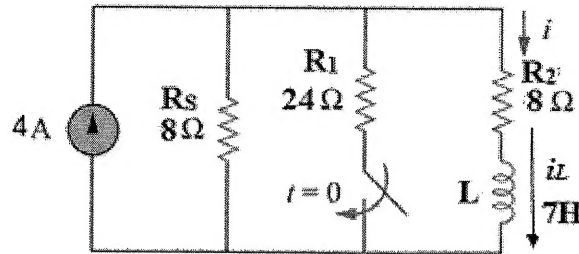


Figure Q4(a)

- (b) A series RLC circuit has  $R = 100\Omega$  and  $C = 3\text{ mF}$ . Determine the value of  $L$  that will make the RLC circuit.

(i) critically damped

[5 marks]

(ii) over damped

[2 marks]

- (c) Design a source free parallel RLC circuit that has the characteristic equation of  $s^2 + 600s + 10^6 = 0$ , assuming  $R = 22k\Omega$ .

[8 marks]

**End of Paper**

## Appendix

Parameter	Series RLC network	Parallel RLC network
Input impedance $Z_{in}$	$R_s + j\omega L_s + \frac{1}{j\omega C_s}$	$\left( \frac{1}{R_p} + \frac{1}{j\omega L_p} + j\omega C_p \right)^{-1}$
Resonance frequency	$\omega_o = \frac{1}{\sqrt{L_s C_s}}$	$\omega_o = \frac{1}{\sqrt{L_p C_p}}$
Quality factor, Q at resonance frequency	$Q_s = \frac{\omega_o L_s}{R_s} = \frac{1}{\omega_o R_s C_s}$	$Q_p = \frac{R_p}{\omega_o L_p} = \omega_o R_p C_p$
Bandwidth BW (note that this is just an approximation)	$\frac{\omega_o}{Q_s}$	$\frac{\omega_o}{Q_p}$

